

Arithmétique 01

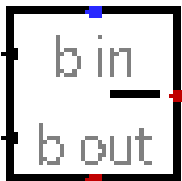
 
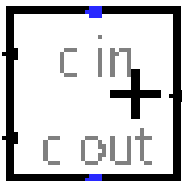


Table des matières


Arithmétique 01.....	1
1) Additionneur 1 bit :.....	3
1-1) Sans la retenue :.....	3
1-2) Avec la retenue de sortie : (ADDSP0 / ADDSP1 / ADDSP2).....	3
1-3 Avec la retenue : (ADD0 / ADD1 / ADD2)......	4
1-4) Sans la retenue de sortie : (ADDSR0 / ADDSR1 / ADDSR2)......	5
1-5) Transistors : (ADDTR)......	5
2) Additionneur :.....	6
2-1) 2 bits :.....	6
2-2) 4 bits :.....	6
2-3) C'est pas sorcier :.....	6
3) Nombre négatif :.....	8
3-1) Binaire :.....	8
3-2) Ne pas faire :.....	8
3-3) Inverseur de signe :.....	8
4) Soustraction 1 bit :.....	9
4-1) Sans la retenue :.....	9
4-2) Avec la retenue de sortie : (SUBSP0 / SUBSP1).....	9
4-3 Avec la retenue : (SUB0 / SUB1).....	10
4-4) Sans la retenue de sortie : (SUBSR0 / SUBSR12)......	11
5) Soustraction :.....	11
5-1) 2 bits :.....	11
5-2) 4 bits :.....	12

1) Additionneur 1 bit :

1-1) Sans la retenue :


Entrée		Sortie
A	B	S
0	0	0
0	1	1
1	0	1
1	1	0
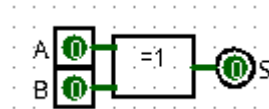
$$\begin{array}{r}
 A \\
 + B \\
 \hline
 = S
 \end{array}
 \quad
 \begin{array}{r}
 0 \\
 + 0 \\
 \hline
 = 0
 \end{array}
 \quad
 \begin{array}{r}
 0 \\
 + 1 \\
 \hline
 = 1
 \end{array}
 \quad
 \begin{array}{r}
 1 \\
 + 0 \\
 \hline
 = 1
 \end{array}
 \quad
 \begin{array}{r}
 1 \\
 + 1 \\
 \hline
 = 0
 \end{array}$$





1-2) Avec la retenue de sortie : (ADDSP0 / ADDSP1 / ADDSP2)

Entrée		Sortie
A	B	RS S
0	0	0
0	1	0
1	0	1
1	1	1

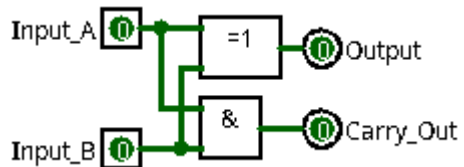

$$\begin{array}{r}
 A \\
 + B \\
 \hline
 = S
 \end{array}
 \quad
 \begin{array}{r}
 0 \\
 + 0 \\
 \hline
 = 0
 \end{array}
 \quad
 \begin{array}{r}
 0 \\
 + 1 \\
 \hline
 = 1
 \end{array}
 \quad
 \begin{array}{r}
 1 \\
 + 0 \\
 \hline
 = 1
 \end{array}
 \quad
 \begin{array}{r}
 1 \\
 + 1 \\
 \hline
 = 0
 \end{array}$$

~~RS~~ 0 0 0 1

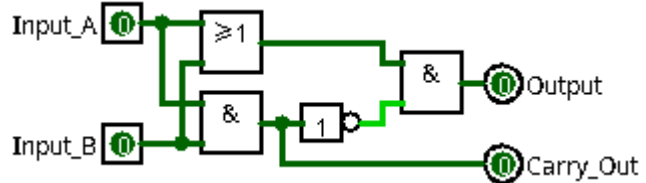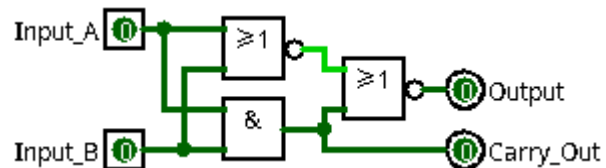

1-3 Avec la retenue : (ADD0 / ADD1 / ADD2)

$\begin{array}{r} R \\ + A \\ + B \\ \hline = S \\ RS \end{array}$	$\begin{array}{r} 0 \\ + 0 \\ + 0 \\ \hline = 0 \\ 0 \end{array}$	$\begin{array}{r} 0 \\ + 0 \\ + 1 \\ \hline = 1 \\ 0 \end{array}$	$\begin{array}{r} 0 \\ + 1 \\ + 0 \\ \hline = 1 \\ 0 \end{array}$	$\begin{array}{r} 0 \\ + 1 \\ + 1 \\ \hline = 0 \\ 1 \end{array}$
$\begin{array}{r} R \\ + A \\ + B \\ \hline = S \\ RS \end{array}$	$\begin{array}{r} 1 \\ + 0 \\ + 0 \\ \hline = 1 \\ 0 \end{array}$	$\begin{array}{r} 1 \\ + 0 \\ + 1 \\ \hline = 0 \\ 1 \end{array}$	$\begin{array}{r} 1 \\ + 1 \\ + 0 \\ \hline = 0 \\ 1 \end{array}$	$\begin{array}{r} 1 \\ + 1 \\ + 1 \\ \hline = 1 \\ 1 \end{array}$

Entrée			Sortie	
R	A	B	RS	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

R	A	B	S	S=
0	0	0	0	0
0	0	1	1	$\bar{R} \cdot \bar{A} \cdot B$
0	1	0	1	$\bar{R} \cdot A \cdot \bar{B}$
0	1	1	0	0
1	0	0	1	$R \cdot \bar{A} \cdot \bar{B}$
1	0	1	0	0
1	1	0	0	0
1	1	1	1	$R \cdot A \cdot B$

R	A	B	RS	RS=
0	0	0	0	0
0	0	1	0	0
0	1	0	0	0
0	1	1	1	$\bar{R} \cdot A \cdot B$
1	0	0	0	0
1	0	1	1	$R \cdot \bar{A} \cdot B$
1	1	0	1	$R \cdot A \cdot \bar{B}$
1	1	1	1	$R \cdot A \cdot B$

Algèbre de Boole

$$S = (\bar{R} \cdot \bar{A} \cdot B) + (\bar{R} \cdot A \cdot \bar{B}) + (R \cdot \bar{A} \cdot \bar{B}) + (R \cdot A \cdot B)$$

$$S = (\bar{R} \cdot \bar{A} \cdot B) + (\bar{R} \cdot A \cdot \bar{B}) + (R \cdot \bar{A} \cdot \bar{B}) + (R \cdot A \cdot B)$$

$$S = \bar{R} \cdot \bar{A} \cdot B + \bar{R} \cdot A \cdot \bar{B} + R \cdot \bar{A} \cdot \bar{B} + R \cdot A \cdot B$$

$$S = \bar{R} \cdot (\bar{A} \cdot B + A \cdot \bar{B}) + R \cdot (\bar{A} \cdot \bar{B} + A \cdot B)$$

$$S = \bar{R} \cdot (A \oplus B) + R \cdot (\bar{A} \oplus \bar{B})$$

$$S = R \oplus (A \oplus B)$$

$$S = (A \oplus B) \oplus R$$

Algèbre de Boole

$$RS = (\bar{R} \cdot A \cdot B) + (R \cdot \bar{A} \cdot B) + (R \cdot A \cdot \bar{B}) + (R \cdot A \cdot B)$$

$$RS = (\bar{R} \cdot A \cdot B) + (R \cdot \bar{A} \cdot B) + (R \cdot A \cdot \bar{B}) + (R \cdot A \cdot B)$$




$$RS = \bar{R} \cdot A \cdot B + R \cdot \bar{A} \cdot B + R \cdot A \cdot \bar{B} + R \cdot A \cdot B$$

$$RS = \bar{R} \cdot A \cdot B + R \cdot \bar{A} \cdot B + R \cdot A \cdot \bar{B} + R \cdot A \cdot B$$

$$RS = (\bar{R} + R) \cdot (A \cdot B) + R \cdot (\bar{A} \cdot B + A \cdot \bar{B})$$

$$RS = 1 \cdot (A \cdot B) + R \cdot (A \oplus B)$$

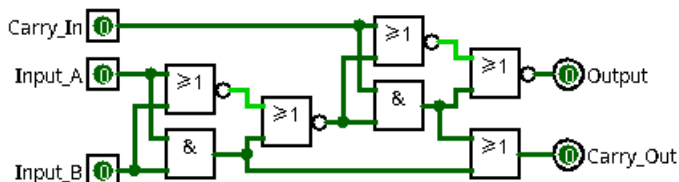
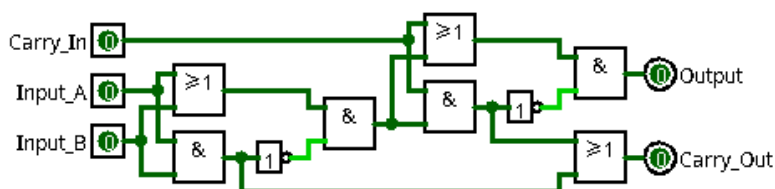
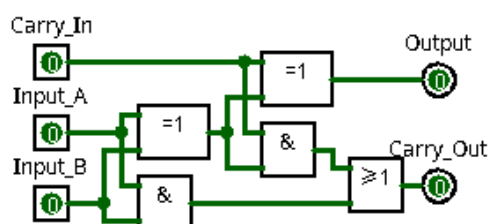
$$RS = (A \cdot B) + ((A \oplus B) \cdot R)$$




1-4) Sans la retenue de sortie : (ADDSR0 / ADDSR1 / ADDSR2)

	R		0		0		0		0
+	A	+	0	+	0	+	1	+	1
+	B	+	0	+	1	+	0	+	1
=	S	=	0	=	1	=	1	=	0

	R		1		1		1		1
+	A	+	0	+	0	+	1	+	1
+	B	+	0	+	1	+	0	+	1
=	S	=	1	=	0	=	0	=	1

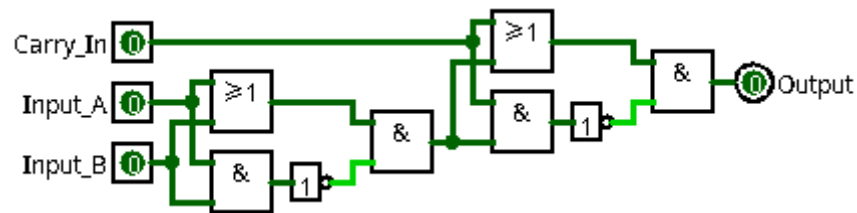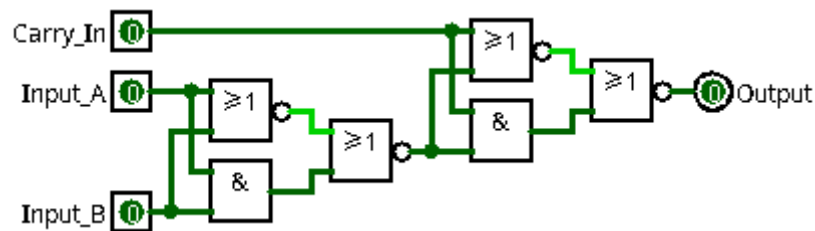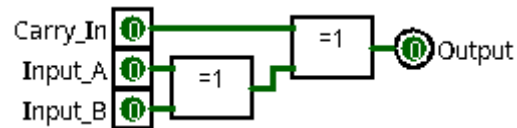


1-5) Transistors : (ADDTR)


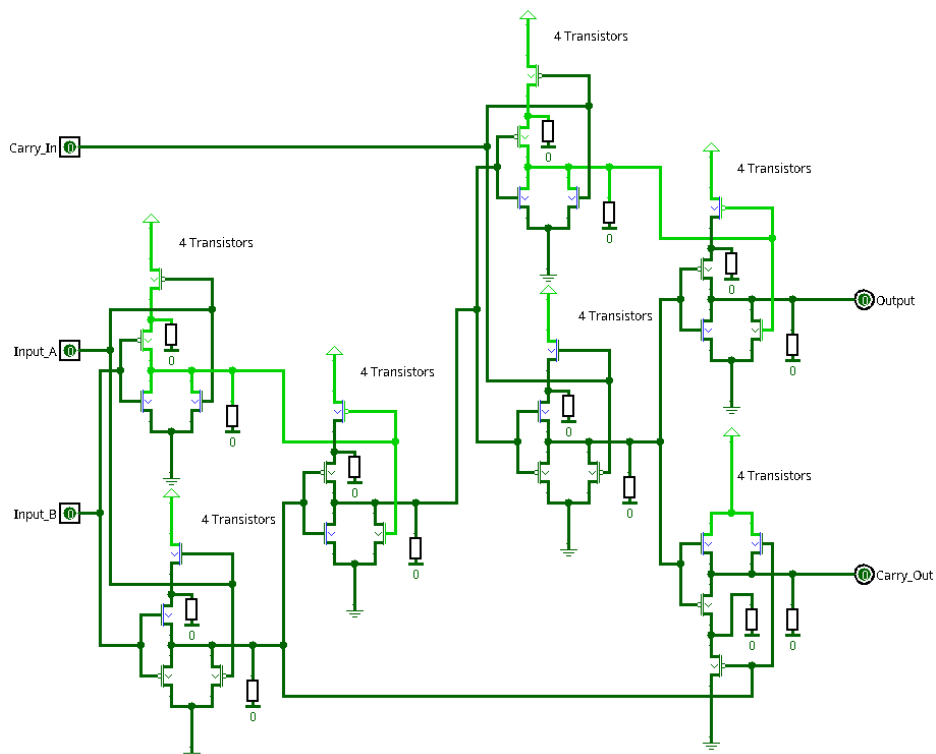


2) Additionneur :



2-1) 2 bits :


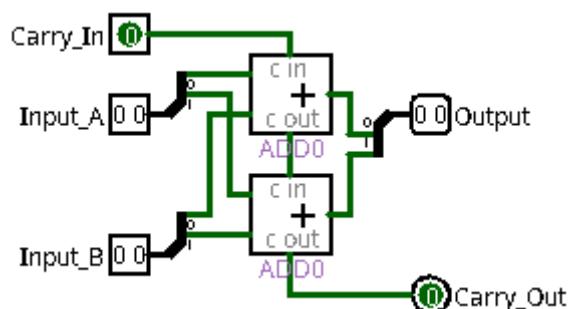


2-2) 4 bits :

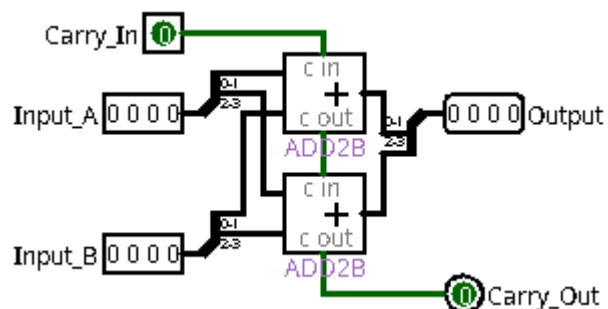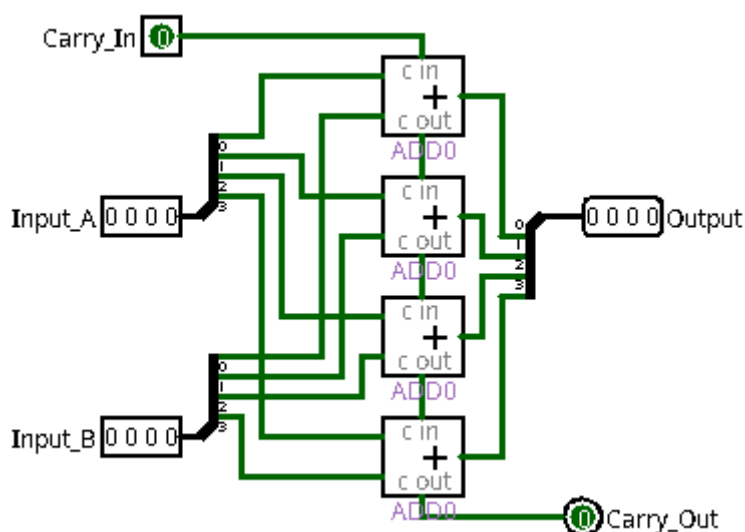

2-3) C'est pas sorcier :

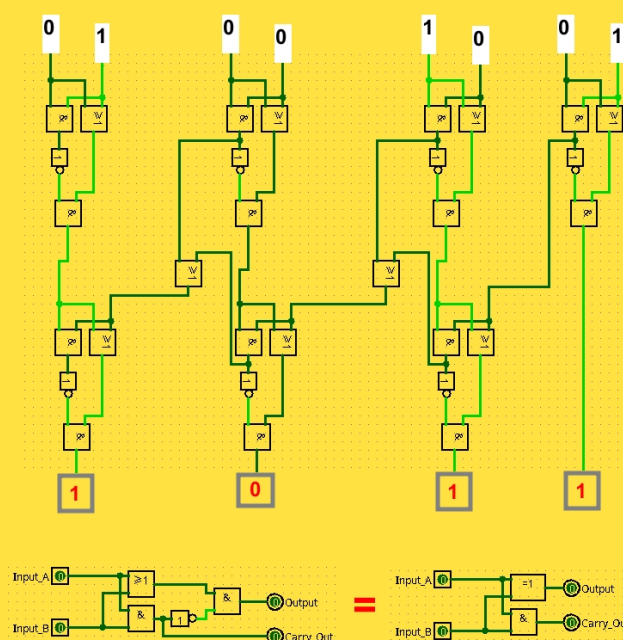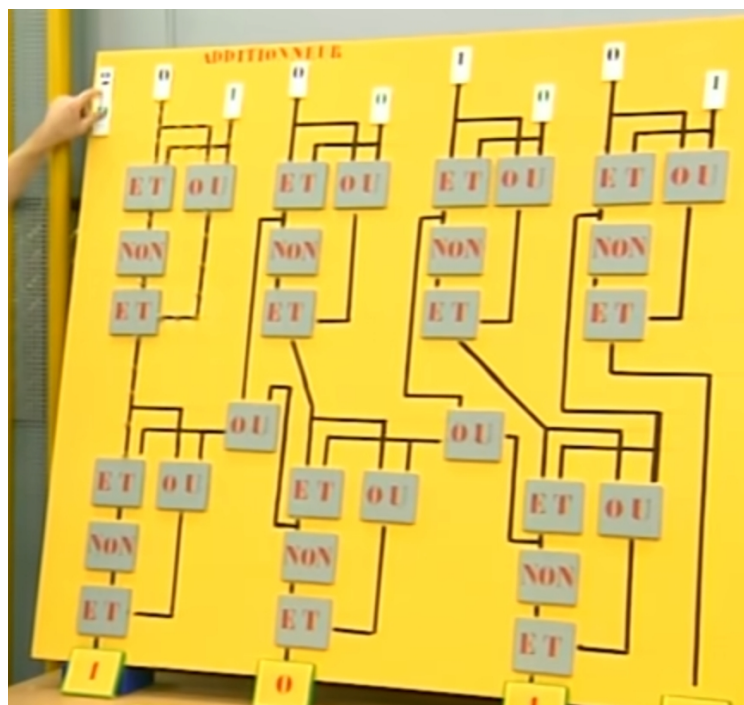

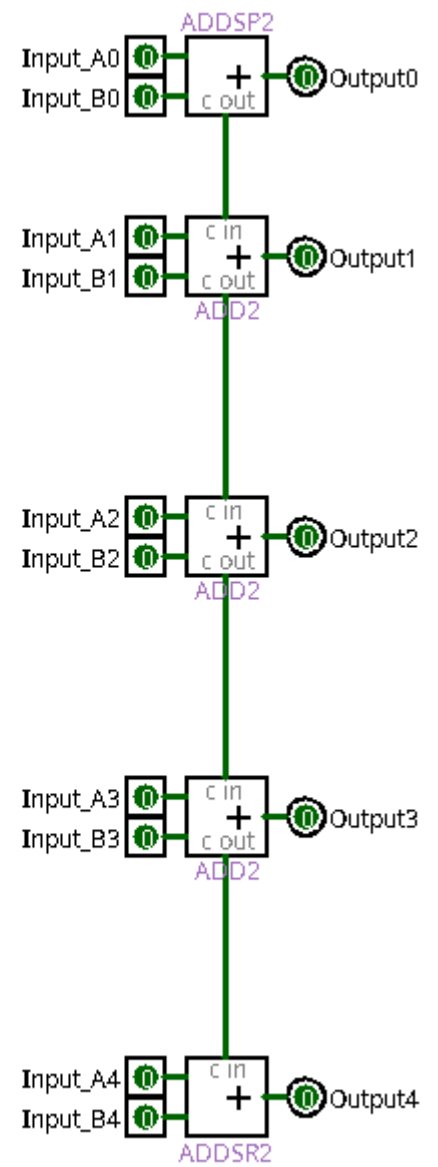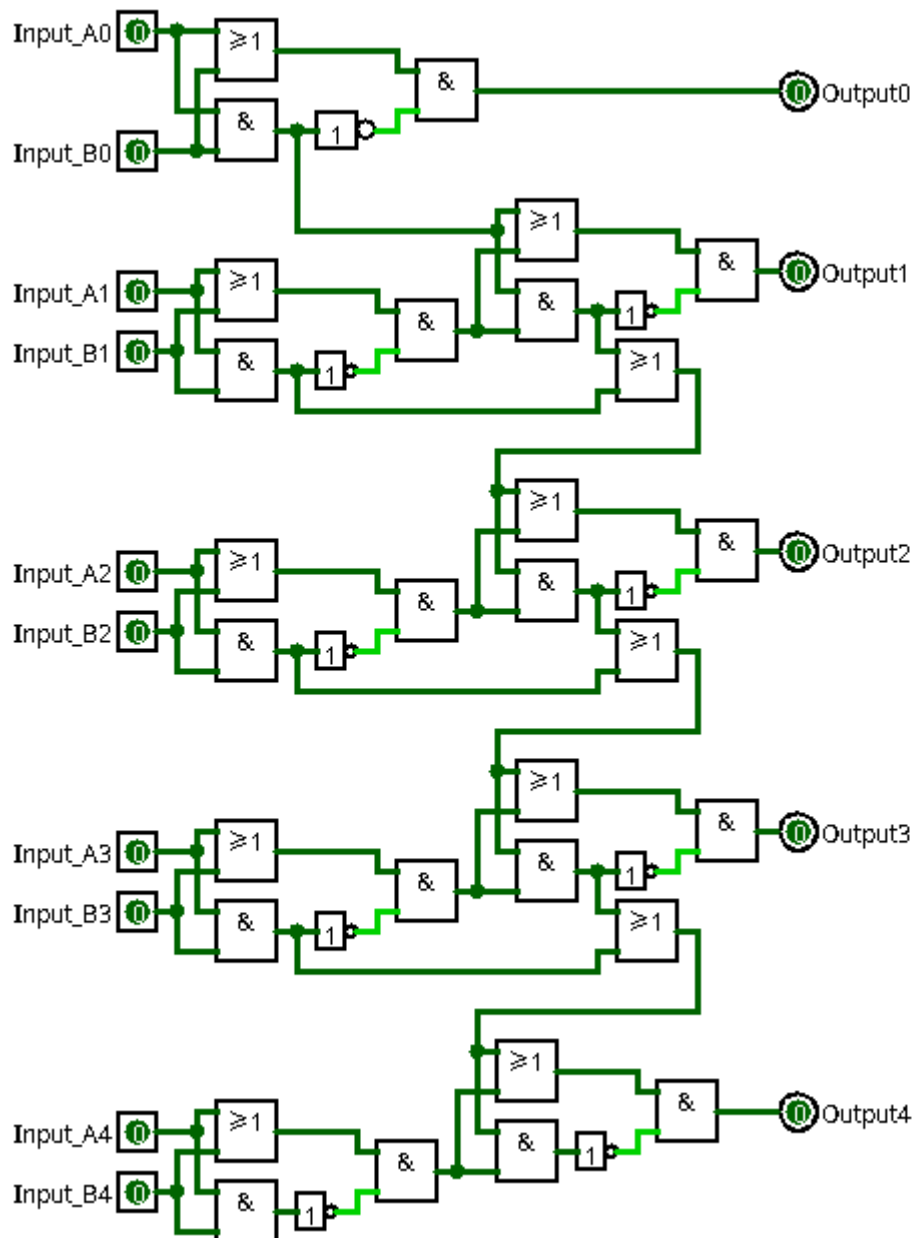

3) Nombre négatif :

3-1) Binaire :



Binaire	Décimal
0 0 0 0	0
0 0 0 1	1
0 0 1 0	2
0 0 1 1	3
0 1 0 0	4
0 1 0 1	5
0 1 1 0	6
0 1 1 1	7
1 0 0 0	-8
1 0 0 1	-7
1 0 1 0	-6
1 0 1 1	-5
1 1 0 0	-4
1 1 0 1	-3
1 1 1 0	-2
1 1 1 1	-1

	0 0 0 1	1
NOT	1 1 1 0	-2
+1	1 1 1 1	-1
	1 1 1 1	-1
NOT	0 0 0 0	0
+1	0 0 0 1	1
	0 1 1 0	6
NOT	1 0 0 1	0
+1	1 0 1 0	-6
	1 0 1 0	-6
NOT	0 1 0 1	5
+1	0 1 1 0	6

3-2) Ne pas faire :

	0 0 0 1	1
+1	0 0 1 0	2
NOT	1 1 0 1	-3
	1 1 1 1	-1
+1	0 0 0 0	0
NOT	0 0 0 1	1
	0 1 1 0	6
+1	0 1 1 1	7
NOT	1 0 0 0	-8
	1 0 1 0	-6
+1	1 0 1 1	-5
NOT	0 1 0 0	4


3-3) Inverseur de signe :

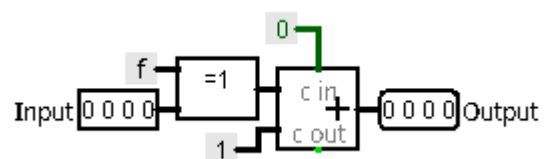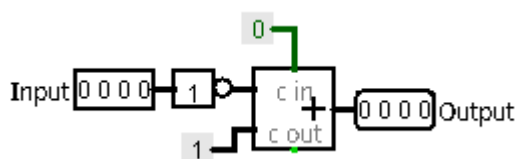


4) Soustraction 1 bit :

4-1) Sans la retenue :


Entrée		Sortie
A	B	S
0	0	0
0	1	1
1	0	1
1	1	0

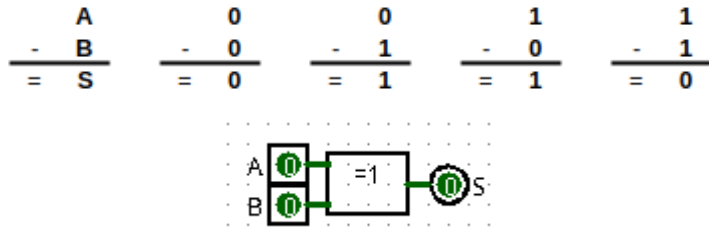

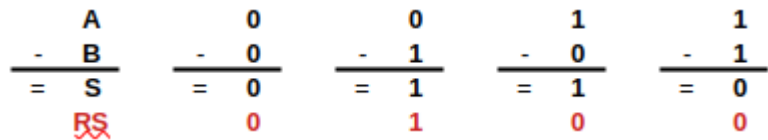4-2) Avec la retenue de sortie : (SUBSP0 / SUBSP1)



Entrée		Sortie	
A	B	RS	S
0	0	0	0
0	1	1	1
1	0	0	1
1	1	0	0

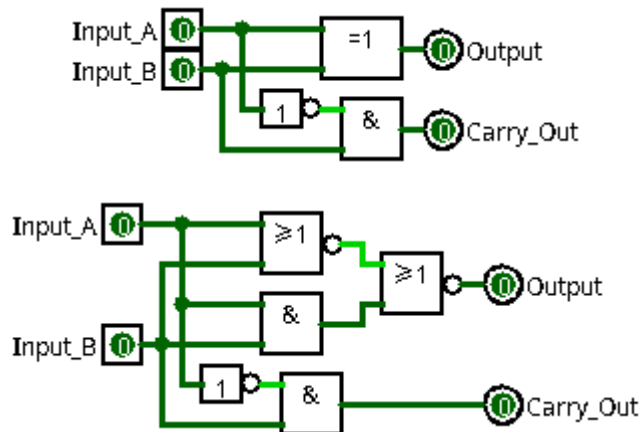

4-3 Avec la retenue : (SUB0 / SUB1)

$\begin{array}{r} A \\ - (R+B) \\ \hline A \\ - (R+B) \\ \hline = S \\ \text{RS} \end{array}$	$\begin{array}{r} 0 \\ - (0+0) \\ \hline 0 \\ - 0 \\ \hline = 0 \\ 0 \end{array}$	$\begin{array}{r} 0 \\ - (0+1) \\ \hline 0 \\ - 1 \\ \hline = 1 \\ 1 \end{array}$	$\begin{array}{r} 1 \\ - (0+0) \\ \hline 1 \\ - 0 \\ \hline = 1 \\ 0 \end{array}$	$\begin{array}{r} 1 \\ - (0+1) \\ \hline 1 \\ - 1 \\ \hline = 0 \\ 0 \end{array}$
$\begin{array}{r} A \\ - (R+B) \\ \hline A \\ - (R+B) \\ \hline = S \\ \text{RS} \end{array}$	$\begin{array}{r} 0 \\ - (1+0) \\ \hline 0 \\ - 1 \\ \hline = 1 \\ 1 \end{array}$	$\begin{array}{r} 0 \\ - (1+1) \\ \hline 0 \\ - 0 \\ \hline = 0 \\ 1 \end{array}$	$\begin{array}{r} 1 \\ - (1+0) \\ \hline 1 \\ - 1 \\ \hline = 0 \\ 0 \end{array}$	$\begin{array}{r} 1 \\ - (1+1) \\ \hline 1 \\ - 0 \\ \hline = 1 \\ 1 \end{array}$

Entrée			Sortie	
R	A	B	RS	S
0	0	0	0	0
0	0	1	1	1
0	1	0	0	1
0	1	1	0	0
1	0	0	1	1
1	0	1	1	0
1	1	0	0	0
1	1	1	1	1

Entrée			Sortie	
R	A	B	S	S=
0	0	0	0	0
0	0	1	1	$\bar{R} \cdot \bar{A} \cdot B$
0	1	0	1	$\bar{R} \cdot A \cdot \bar{B}$
0	1	1	0	0
1	0	0	1	$R \cdot \bar{A} \cdot \bar{B}$
1	0	1	0	0
1	1	0	0	0
1	1	1	1	$R \cdot A \cdot B$

Entrée			Sortie	
R	A	B	RS	RS=
0	0	0	0	0
0	0	1	1	$\bar{R} \cdot \bar{A} \cdot B$
0	1	0	0	0
0	1	1	0	0
1	0	0	1	$R \cdot \bar{A} \cdot \bar{B}$
1	0	1	1	$R \cdot \bar{A} \cdot B$
1	1	0	0	0
1	1	1	1	$R \cdot A \cdot B$

Algèbre de Boole

$$S = \bar{A} \cdot \bar{R} \cdot B + \bar{A} \cdot R \cdot \bar{B} + A \cdot \bar{R} \cdot \bar{B} + A \cdot R \cdot B$$


$$S = \bar{A} \cdot \bar{R} \cdot B + \bar{A} \cdot R \cdot \bar{B} + A \cdot \bar{R} \cdot \bar{B} + A \cdot R \cdot B$$

$$S = \bar{A} \cdot (\bar{R} \cdot B + R \cdot \bar{B}) + A \cdot (\bar{R} \cdot \bar{B} + R \cdot B)$$

$$S = \bar{A} \cdot (R \oplus B) + A \cdot (\bar{R} \oplus \bar{B})$$

$$S = A \oplus (R \oplus B)$$

$$S = (R \oplus B) \oplus A$$

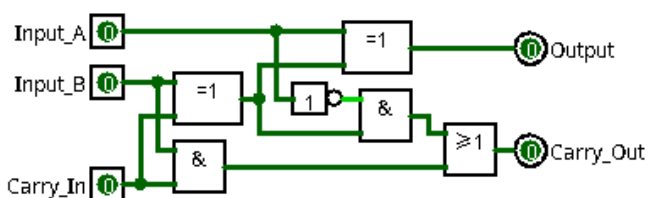

Algèbre de Boole

$$RS = \bar{A} \cdot \bar{R} \cdot B + \bar{A} \cdot R \cdot \bar{B} + \bar{A} \cdot R \cdot B + A \cdot R \cdot B$$


$$RS = \bar{A} \cdot \bar{R} \cdot B + \bar{A} \cdot R \cdot \bar{B} + \bar{A} \cdot R \cdot B + A \cdot R \cdot B$$

$$RS = \bar{A} \cdot (\bar{R} \cdot B + R \cdot \bar{B}) + (\bar{A} + A) \cdot (R \cdot B)$$

$$RS = \bar{A} \cdot (B \oplus R) + 1 \cdot (R \cdot B)$$


$$RS = \bar{A} \cdot (B \oplus R) + (R \cdot B)$$
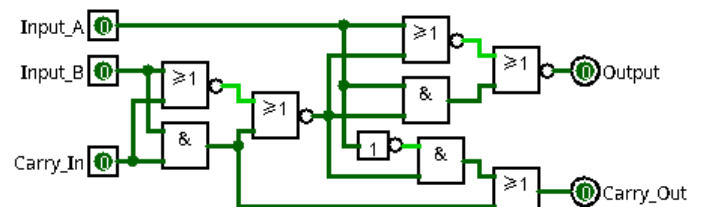
$$RS = (R \cdot B) + ((B \oplus R) \cdot \bar{A})$$




4-4) Sans la retenue de sortie : (SUBSR0 / SUBSR12)

$\begin{array}{r} A \\ - (R+B) \\ \hline A \\ - (R+B) \\ \hline = S \end{array}$	$\begin{array}{r} 0 \\ - (0+0) \\ \hline 0 \\ - 0 \\ \hline = 0 \end{array}$	$\begin{array}{r} 0 \\ - (0+1) \\ \hline 0 \\ - 1 \\ \hline = 1 \end{array}$	$\begin{array}{r} 1 \\ - (0+0) \\ \hline 1 \\ - 0 \\ \hline = 1 \end{array}$	$\begin{array}{r} 1 \\ - (0+1) \\ \hline 1 \\ - 1 \\ \hline = 0 \end{array}$
$\begin{array}{r} A \\ - (R+B) \\ \hline A \\ - (R+B) \\ \hline = S \end{array}$	$\begin{array}{r} 0 \\ - (1+0) \\ \hline 0 \\ - 1 \\ \hline = 1 \end{array}$	$\begin{array}{r} 0 \\ - (1+1) \\ \hline 0 \\ - 0 \\ \hline = 0 \end{array}$	$\begin{array}{r} 1 \\ - (1+0) \\ \hline 1 \\ - 1 \\ \hline = 0 \end{array}$	$\begin{array}{r} 1 \\ - (1+1) \\ \hline 1 \\ - 0 \\ \hline = 1 \end{array}$

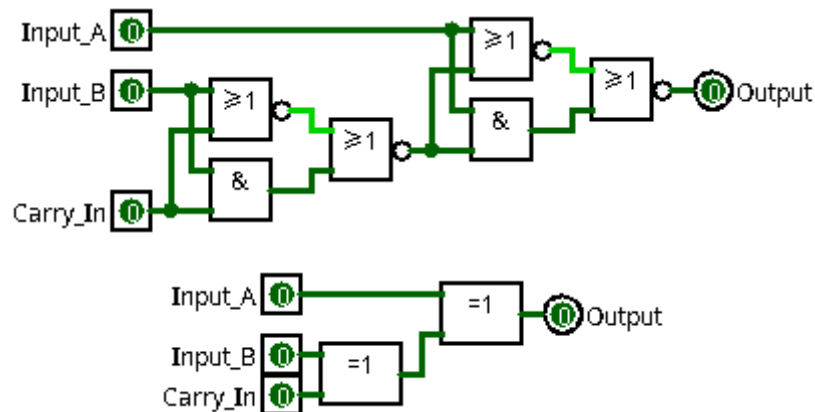

5) Soustraction :

5-1) 2 bits :

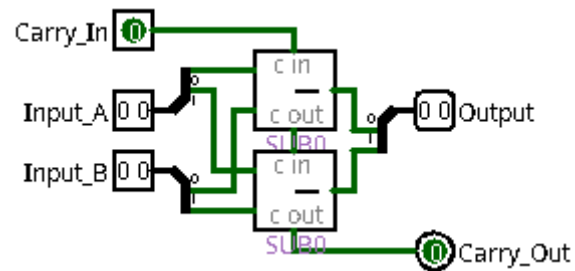

5-2) 4 bits :

